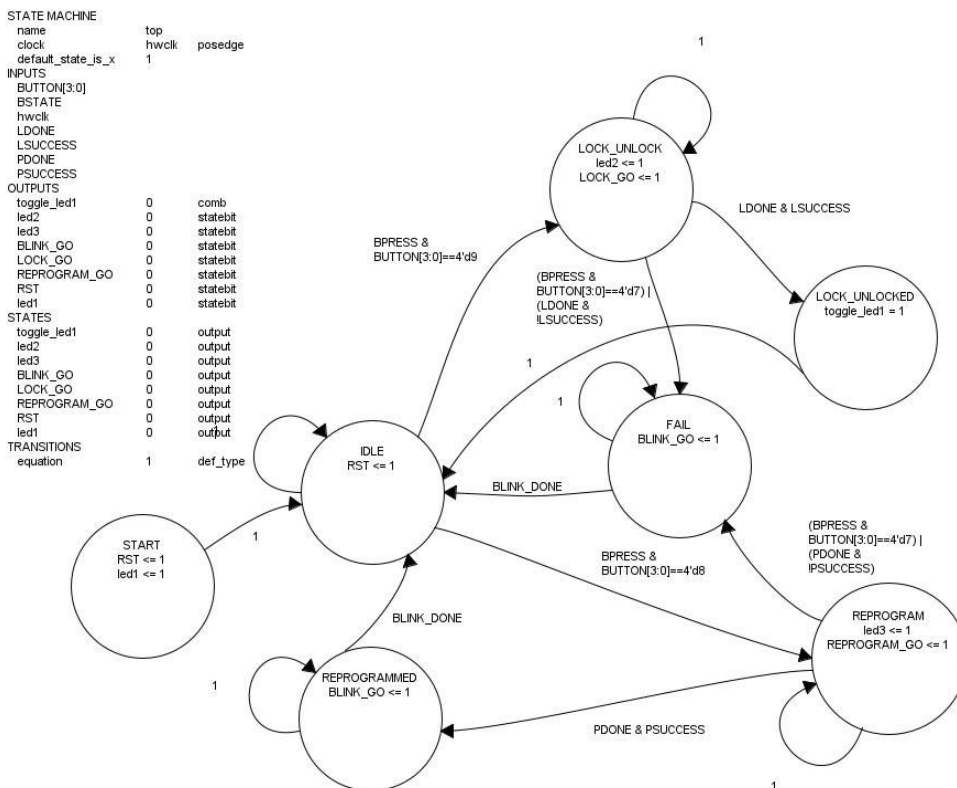


## FPGA Project Report

For my implementation of the FPGA project, I included five primary FSMs, three of which include datapaths. In addition to these, I had three smaller helper modules and the provided Button\_code modules.

At the highest level of the hierarchy, the top module directs the flow of the entire system. It consists of seven states: START, IDLE, LOCK\_UNLOCK, LOCK\_UNLOCKED, REPROGRAM, REPROGRAMMED, and REPROGRAMMED. The machine begins in the START state, where registers and values are initialized, as is led1, which represents the lock/unlock state of the machine. From here, the machine immediately transitions to the IDLE state, where it waits for input. If it receives a nine, it will go to the LOCK\_UNLOCK state, where the user inputs a UC. A control signal is sent to an instance of the enter\_code module and the machine remains in the state until a status signal is received back. LED2 is also lit. If the user inputs the correct UC, the LOCK\_UNLOCKED state is reached, where the led is toggled and the machine returns to IDLE. If the user fails, the FAIL state is reached, where the blink module is told to blink 0.5 seconds off, 1 second on three times. After this has been completed, it returns to the IDLE state. From the IDLE state, if an eight is received, the REPROGRAM state is reached, where LED3 is lit, and the REPROGRAM module will run. It will check for the PC, then accept a new UC and check the second UC against the first. Success will lead to REPROGRAMMED, where the BLINK module is made to blink on for 0.2 and off for 0.2 seconds, five times. Failure will lead to the FAIL state. The inputs and outputs of the module primarily deal with the hardware itself, such as the keypad rows and columns, the hardware clock, and the LEDs. The top module also contains the enterDigits module, which was provided, and outputs the current BUTTON, and where it is pressed, BSTATE. This latter signal is put through a synchronizer to obtain BPRESS, which goes high after the falling edge of BSTATE, which corresponds to a button being released. Although the top module doesn't have a RST, it asserts RST on the other modules when it is in the START and IDLE states.




```
input hwclk;

output keypad_r1;
output keypad_r2;
output keypad_r3;
input keypad_c1;
input keypad_c2;
input keypad_c3;

output led1;
output led2;
output led3;
```

The blink module is relatively simple. It consists of three states: START, COUNTING, and COMPLETE. It remains in the START state until given the GO signal from the top module, at which point it transitions to the COUNTING state, where it activates the module's datapath. Once the datapath has run, the COMPLETE state is reached and DONE is asserted, allowing the top module to continue running. The datapath is basically just a counter. It is incremented by one every clock edge, and the status of the LED changes based on its value. The datapath inputs ON, and OFF specify the number of deciseconds that the LED should remain on and off, respectively. The REPEAT input specifies how many times the LED should blink before turning off. These signals are dependent on the top module's state, which also controls which LED is assigned the output LED. I chose to go with the interpretation that led2 blinks if led2 is on when the FAIL state is incurred, and led3 blinks if led3 is on. GO, and C\_DONE are status signals.

 

```


input CLK;
input RST;
input GO;
input[4:0] ON;
input[4:0] OFF;
input[2:0] REPEAT;

output DONE;
output LED;
reg C_DONE;
  
```

The enter\_code module is used twice, in the top and reprogram modules. It follows the general structure for a digital lock laid out in discussion and the textbook. It has five states: START, ENTER, WAIT, INCORRECT, and CORRECT. It communicates with its parent module with GO, SUCCESS and DONE. When GO is asserted, the machine transitions to the ENTER state. This is where the datapath portion of this module comes in. If BPRESS is high, BUTTON is compared against the four most significant bits of CORRECT\_CODE, which is left-shifted by four at each button press. An index is also kept, and two signals keep track of whether the keys and lengths of the input and code are equal. These two signals are called kmatch and match, respectively. Because this module is used for the UC unlock and the UC reprogramming, an input named ENTER\_BUTTON is required, which is 4'd9 in the prior case and 4'd8 in the latter. If at a button press, the button doesn't match the current code, it goes to a wait state where it waits for the ENTER\_BUTTON to be pressed, where it then moves to INCORRECT. If the lengths don't match, the machine also goes here. But, if the input matches all of CORRECT\_CODE, it goes to the CORRECT state, where DONE and SUCCESS are true. The datapath is where two of the smaller modules play a role. The counter module keeps a three bit counter. Whenever a valid BUTTON is pressed when the machine is in the ENTER state, the index is incremented. This index signal is used in

the codeReg to get the corresponding integer from CORRECT\_CODE, starting from zero at the MSB of CORRECT\_CODE. This is output on current\_button.

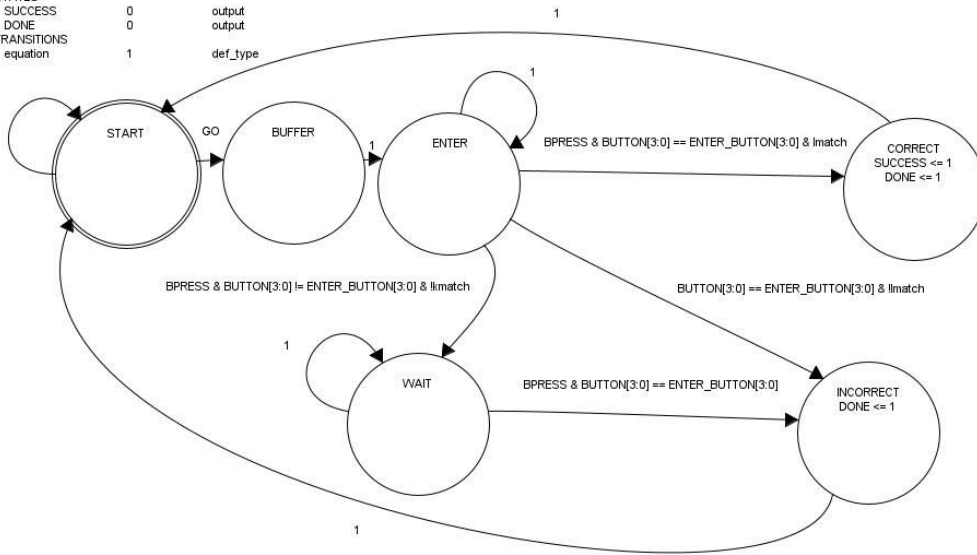STATE MACHINE  
 name enter\_code  
 clock CLK posedge  
 reset\_signal RST positive  
 reset\_state START anyvalue  
 default\_state\_is\_x 1  
 INPUTS  
 CLK  
 RST  
 BUTTON[3:0]  
 BSTATE  
 GO  
 OUTPUTS  
 SUCCESS 0 statebit  
 DONE 0 statebit  
 STATES  
 SUCCESS 0 output  
 DONE 0 output  
 TRANSITIONS  
 equation 1 def\_type



```

input CLK;
input RST;
input GO;
input[3:0] BUTTON;
input BPRESS;
input[23:0] CORRECT_CODE;
input[2:0] LENGTH;
input[3:0] ENTER_BUTTON;

output SUCCESS;
output DONE;
  
```

```

input clk;
input rst;
input inc;

output[2:0] index;
  
```

```

input clk;
input rst;
input[23:0] code;
input[2:0] index;
input[2:0] length;

output[3:0] current_button;
  
```

The reprogram module contains one enter\_code module and one enter\_new\_code module. It has six states: START, ENTER\_PC, ENTER\_UC1, ENTER\_UC2, COMPLETE, and FAILURE. The same module is used for the ENTER\_PC and ENTER\_UC2 states. It is reset and loaded with new inputs for ENTER\_UC2. GO, DONE, and SUCCESS are the control signals between top and reprogram, and NEWCODE and NEWLENGTH contain the value that UC is updated to if the COMPLETE state is reached.

STATE MACHINE

name	reprogram	
clock	CLK	posedge
reset_signal	RST	positive
reset_state	START	anyvalue
default_state_is_x	1	

INPUTS

GO	CLK	RST	CODE_DONE	CODE_SUCCESS	NEW_DONE	NEW_SUCCESS
0	0	0	0	0	0	0

OUTPUTS


DONE	SUCCESS	CODE_GO	NEW_GO
0	0	0	0

STATES

DONE	SUCCESS	CODE_GO	NEW_GO
0	0	0	0

TRANSITIONS

equation	def_type
1	def_type

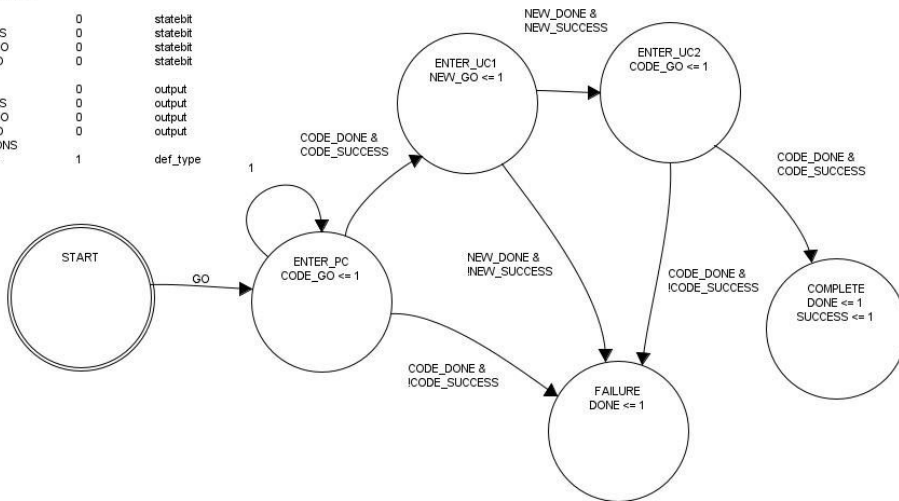


```

input CLK;
input RST;
input GO;
input[23:0] PC;
input[2:0] PC_LENGTH;
input[23:0] UC;
input[2:0] UC_LENGTH;
input[3:0] BUTTON;
input BPRESS;

output DONE;
output SUCCESS;
output[23:0] NEWCODE;
output[2:0] NEWLENGTH;

```

The enter\_new\_code module is for inputting a new UC to the system. It's state diagram is almost identical to that of enter\_code, except that kmatch and lmatch are replaced by kvalid and lvalid, where are used to determine whether the inputted code is a valid UC. The datapath implementation is therefore different, and it uses a module called newCodeReg. This takes in the current BUTTON press as input, as well as shift, a signal that tells the module whether a valid button press is taking place, and whether the current state is ENTER. If so, newCodeReg left shifts its stored code and increments its index. This code is wired to the output of the enter\_new\_code module, which is in turn wired to the output of the reprogram module. GO, DONE, and SUCCESS are control signals.

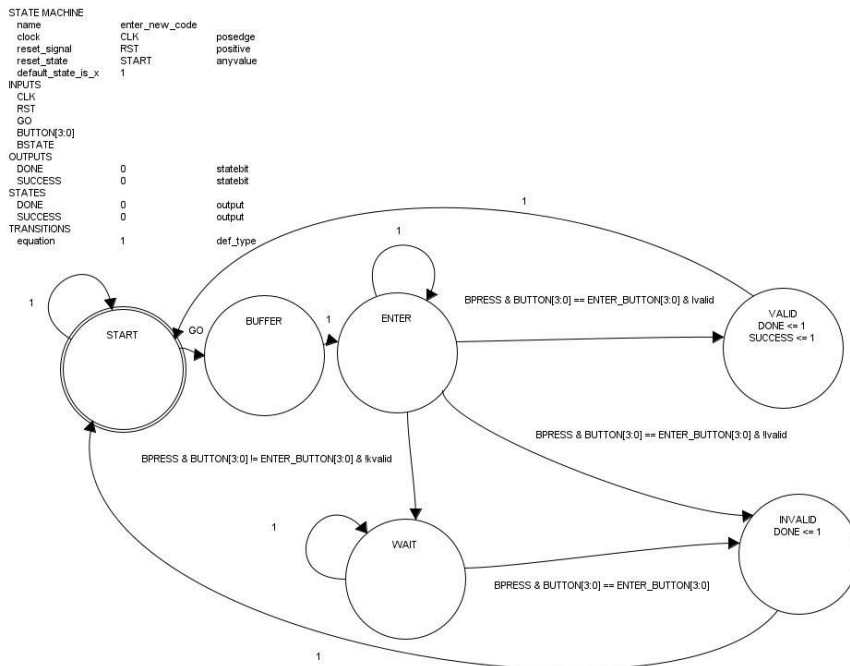

```

input CLK;
input RST;
input GO;
input[3:0] BUTTON;
input BPRESS;
input[3:0] ENTER_BUTTON;

output SUCCESS;
output DONE;
output[23:0] NEWCODE;
output[2:0] NEWLENGTH;
  
```

```


input clk;
input rst;
input[3:0] button;
input shift;

output[23:0] newcode;
output[2:0] length;
  
```






 Pictured above is an example timing diagram for the top module, with some of its inputs, outputs, and control signals. As the blink module has not been used yet, its output is red. First, the lock is unlocked, which toggles led1. After that, the code is reprogrammed, which can be seen by the change in UC[23:0] at the yellow line to the right of the diagram.



 This is a close-up of the enter\_code unlock portion of the larger time diagram. Notice the simultaneous raising of LDONE and LSUCCESS to indicate the correct UC was entered.



This is a close-up of the reprogramming portion of the larger time diagram. Notice the simultaneous raising of PDONE and PSUCCESS, as well as the changing of UC and UC\_LENGTH and ON and OFF, to indicate success.

The PC can be changed in the top module. It is a parameter, as is its length, PC\_LENGTH. PC is a concatenation of six four bit integers, which can be changed. PC\_LENGTH is a three bit integer and must be specified for the lock to work correctly. For PCs less than six integers, right-justify the integers, so the most significant bits are don't-cares, or random values.

As I did not work with a partner, I did all the work on this project.